


## Electronic Devices and Circuit Theory (Eleventh Edition)

### Soal-soal Bab 4 : DC Biasing—BJTs

Kerjakan di kertas folio bergaris.

2. Given the information appearing in Fig. 4.119, determine:

- $I_C$ .
- $R_C$ .
- $R_B$ .
- $V_{CE}$ .

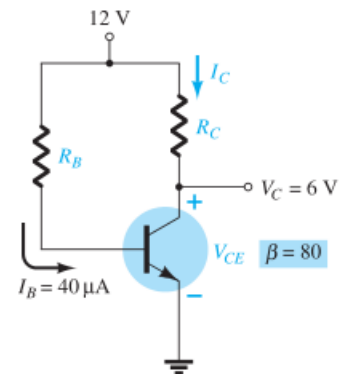


**FIG. 4.119**

Problem 2.

8. For the emitter-stabilized bias circuit of Fig. 4.122, determine:

- $I_{BQ}$ .
- $I_{CQ}$ .
- $V_{CEQ}$ .
- $V_C$ .
- $V_B$ .
- $V_E$ .


g. Gambarkan Garis Beban DC dan titik kerjanya (Qpoint)

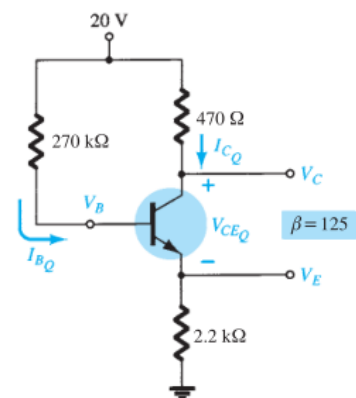

**FIG. 4.122**

17. Given the information provided in Fig. 4.126, determine:


- $I_C$ .
- $V_E$ .
- $V_B$ .
- $R_1$ .

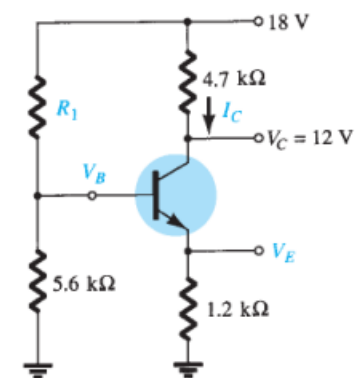

**FIG. 4.126**

29. For the voltage feedback network of Fig. 4.130, determine:

- $I_C$ .
- $V_C$ .
- $V_E$ .
- $V_{CE}$ .

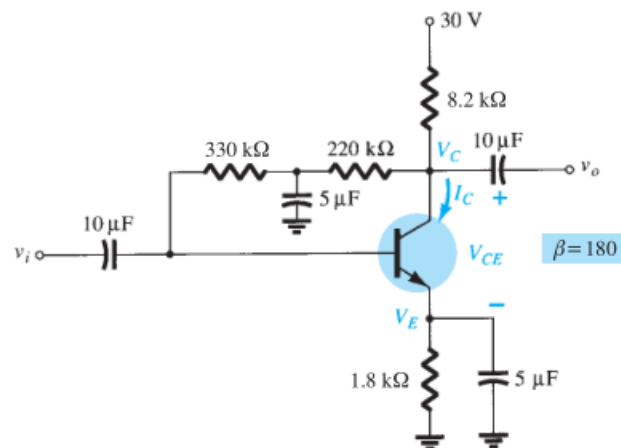


**FIG. 4.130**

Problems 29 and 30.

35. For the emitter follower network of Fig. 4.135

- Find  $I_B$ ,  $I_C$ , and  $I_E$ .
- Determine  $V_B$ ,  $V_C$ , and  $V_E$ .
- Calculate  $V_{BC}$  and  $V_{CE}$ .

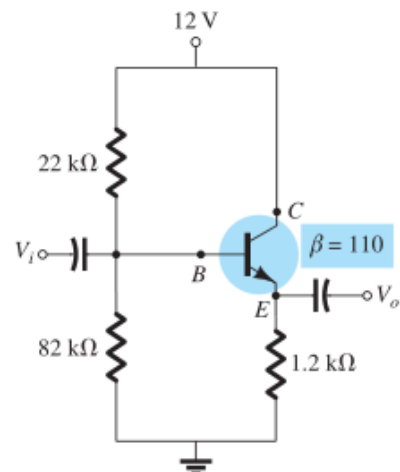


**FIG. 4.135**

Problem 35.

38. For the common-base network of Fig. 4.138


- Using the information provided determine the value of  $R_C$ .
- Find the currents  $I_B$  and  $I_E$ .
- Determine the voltages  $V_{BC}$  and  $V_{CE}$ .

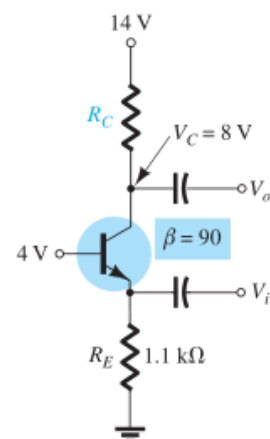

**FIG. 4.138**

Problem 38.

- \*58. Design the transistor inverter of Fig. 4.154 to operate with a saturation current of 8 mA using a transistor with a beta of 100. Use a level of  $I_B$  equal to 120% of  $I_{B_{\max}}$  and standard resistor values.

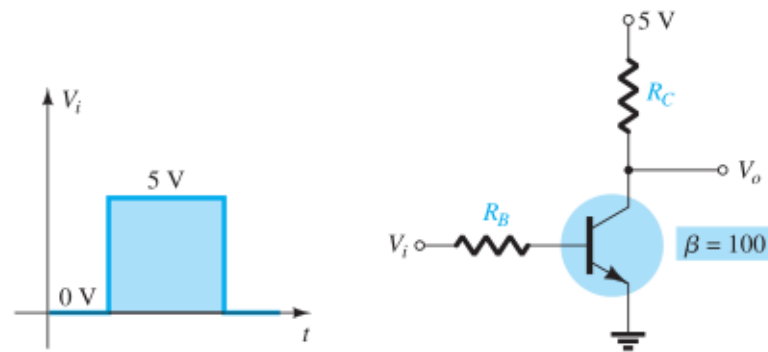

**FIG. 4.154**

Problem 58.