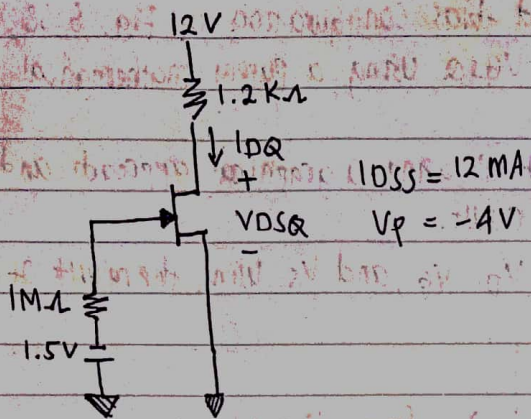


NAMA : SAYID HUSEINI ELFAZIZI
 KELAS : TT-43-11
 NIM : 1101194232

No. _____

Date : _____

1.



for the fixed-bias configuration of fig. 6.67

- sketch the transfer characteristics of the device
- superimpose the network equation on the same graph
- Determine IDQ and $VDSQ$
- Using Shockley's equation, solve for IDQ and then find $VDSQ$, compare with the solution of part (c).

a.) Use the Shorthand method


$V_{GS} (V)$ $ID (mA)$

0 $ID_{SS} = 12$


$0.3 V_P = -1.2$ $\frac{ID_{SS}}{2} = 6$

$0.5 V_P = -2$ $\frac{ID_{SS}}{4} = 3$

$V_P = -4$ 0

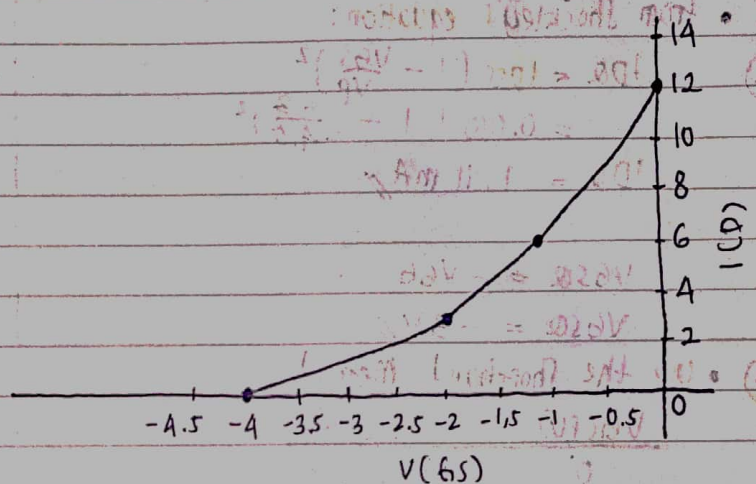

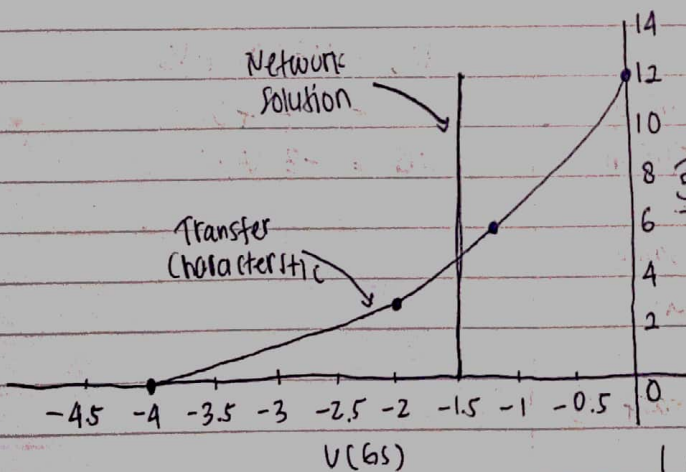b.) for the given network, $V_{GS} = 1.5 V$, therefore



c.) from the intersection on figure 2

$$IDQ = 4.7 \text{ mA}$$

for the given network, $VDSQ$ is given by

$$\begin{aligned} VDSQ &= VDD - IDQ \cdot RD \\ &= 12 - 4.7 \times 1.2 \\ VDSQ &= 6.36 \text{ V} \end{aligned}$$

d.) Recall Shockley's equation


$$\begin{aligned} IDQ &= ID_{SS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \\ &= 0.012 \left(1 - \frac{-1.5}{-4} \right)^2 \end{aligned}$$

$$IDQ = 4.6875 \text{ mA} \quad \text{almost same as part (c)}$$

Since $VDSQ$ is given by,

$$\begin{aligned} VDSQ &= VDD - IDQ \cdot RD \\ &= 12 - 4.6875 \times 1.2 \\ VDSQ &= 6.375 \text{ V} \end{aligned}$$

2.1

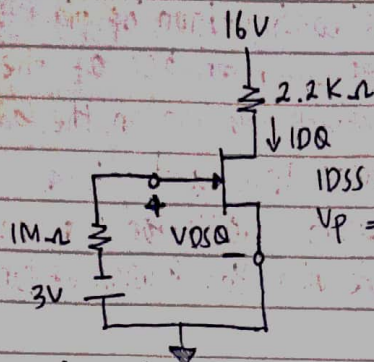

for the fixed-bias configuration of Fig. 6.68, Det:

- I_{DQ} and V_{GSQ} using a purely mathematical approach
- Repeat part (a) using a graphical approach and compare result.
- Find V_{DS} , V_D , V_G , and V_S using the result of part (a)

• from Shockley's equation:

$$\begin{aligned} a.) \quad I_{DQ} &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \\ &= 0.010 \left(1 - \frac{-3}{-4.5}\right)^2 \\ I_{DQ} &= 1.11 \text{ mA} // \end{aligned}$$

$$V_{GSQ} = -V_{GG}$$

$$V_{GSQ} = -3 \text{ V} //$$

b.) • Use the Shorthand Method


$V_{GS}(\text{V})$	$I_D(\text{mA})$
0	$I_{DSS} = 10$
$0.3V_P = -1.35$	$\frac{I_{DSS}}{2} = 5$
$0.5V_P = -2.25$	$\frac{I_{DSS}}{4} = 2.5$
$V_P = -4.5$	0

Sketch the transfer characteristics curve using the evaluated data with the network solution superimposed, from the sketched curve,

$$I_{DQ} = 1.15 \text{ mA} \rightarrow \text{almost the same as part (a)}$$

$$V_{GSQ} = -V_{GG}$$
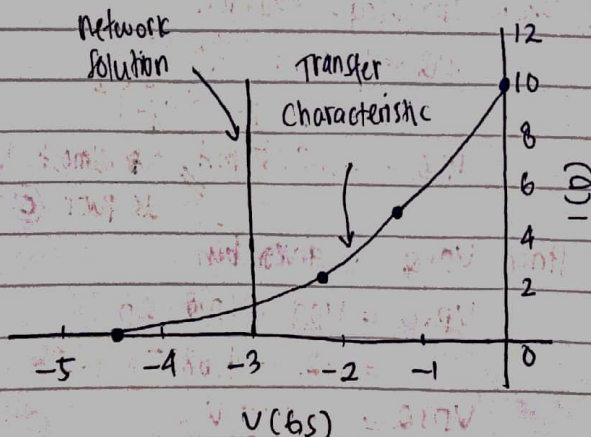
$$V_{GSQ} = -3 \text{ V} \rightarrow \text{the same as part (a)}$$



c.) • from the network,

$$\begin{aligned} V_{DS} &= V_{DD} - I_D R_D \\ &= 16 - (1.11 \times 10^{-3})(2200) \end{aligned}$$

$$V_{DS} = 13.56 \text{ V} //$$

Since the source is connected to the ground, thus $V_S = 0 \text{ V} //$


$$\begin{aligned} V_D &= V_{DS} + V_S \\ &= 13.56 + 0 \end{aligned}$$

$$V_D = 13.56 \text{ V} //$$

$$\begin{aligned} V_G &= V_{GSQ} + V_S \\ &= -3 + 0 \end{aligned}$$

$$V_G = -3 \text{ V} //$$

3.7

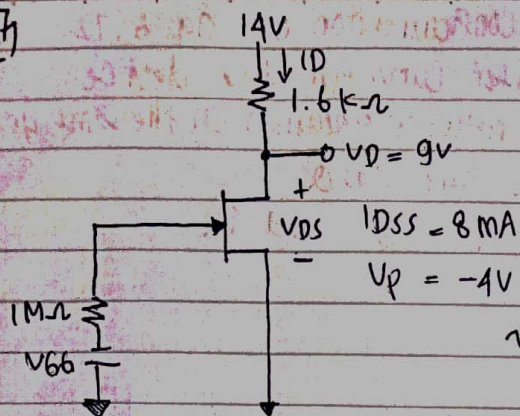Given the measured value of V_D in fig. 6.69,a.) I_D b.) V_{DS} c.) V_{GS}

$$\rightarrow a.) I_D = \frac{V_{DD} - V_D}{R_D} = \frac{14 - 9}{1600} = 3.125 \text{ mA} //$$

$$b.) V_{DS} = V_D - V_S$$

Since $V_S = 0 \text{ V}$ as it is connected to the ground,

$$V_{DS} = 6 - 0$$

$$V_{DS} = 6 \text{ V} //$$

$$c.) I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$


$$3.125 \times 10^{-3} = 0.008 \left(1 - \frac{V_{GS}}{-4}\right)^2$$

$$V_{GS} = -1.5 \text{ V}$$

$$V_{GS} = -V_{GG}$$

$$V_{GG} = 1.5 \text{ V} //$$

4.7

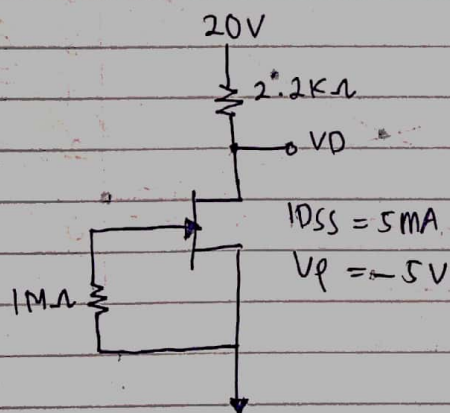Determine V_D for the fixed-bias Configuration of fig. 6.70.

$$\rightarrow V_{GS} = 0$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$= 0.005 \left(1 - \frac{0}{-5}\right)^2$$

$$= 5 \text{ mA} //$$

$$V_D = V_{DD} - I_D \cdot R_D$$

$$= 20 - (0.005)(2200)$$

$$V_D = 9 \text{ V} //$$

Determine V_D for the fixed-bias Configuration of fig. 6.71.

$$\rightarrow V_{GS} = -4 \text{ V}$$


Since $V_{GS} \leq V_p$, $I_D = 0 \text{ mA}$

$$V_D = V_{DD} - I_D \cdot R_D$$


$$= 18 - (0) \cdot (2000)$$

$$V_D = 18 \text{ V} //$$

6.7

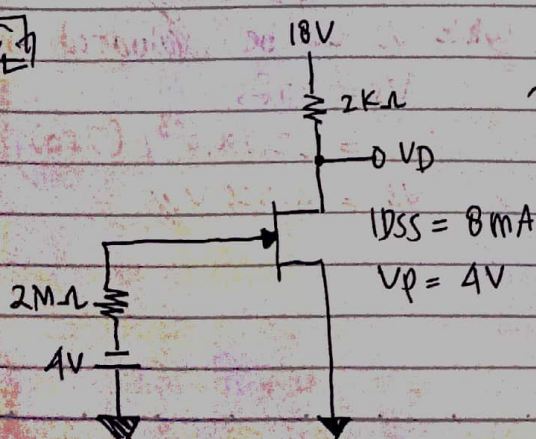


6.1

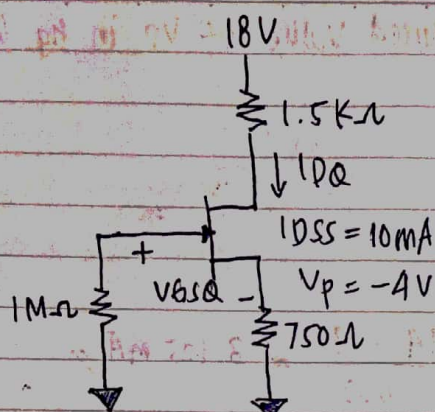

- for the self-bias configuration of Fig. 6.72
- Sketch the transfer curve for the device
 - Superimpose the network equation on the same graph
 - Determine I_{DQ} and V_{GSQ}
 - Calculate V_{DS} , V_D , V_G , and V_S

a) Use the shorthad method

$V_{GS} (V)$	$I_D (mA)$
0	$I_{DSS} = 10$
$0.3 V_P = -1.2$	$\frac{I_{DSS}}{2} = 5$
$0.5 V_P = -2$	$\frac{I_{DSS}}{4} = 2.5$
$V_P = -4$	0

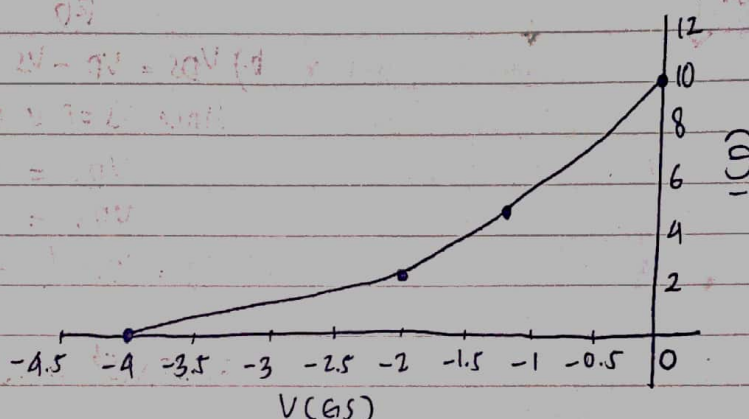


- b) for the given network, the network equation line can be defined by two points, first of which is the origin. The second point can be evaluated from the network equation,

$$V_{GS} = -I_D \cdot R_S$$

for $I_D = 4 \text{ mA}$,
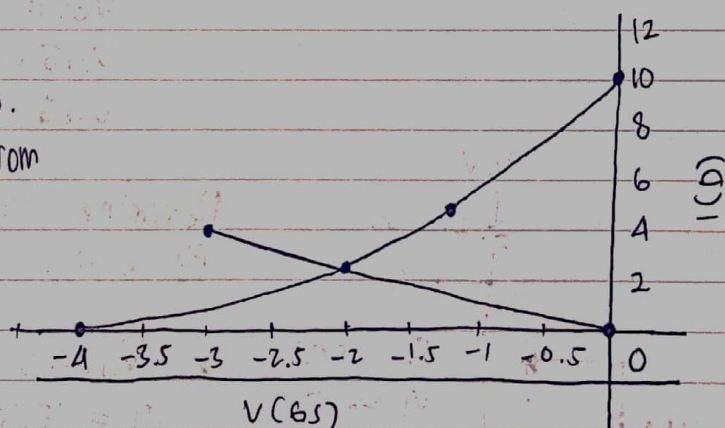
$$V_{GS} = -(0.004)(750) = -3 \text{ V} //$$



- c) from the intersection on figure 2,

$$I_{DQ} = 2.7 \text{ mA} //$$

$$V_{GSQ} = -1.9 \text{ V} //$$

- d) $V_{DS} = V_D - V_S$

$$= (V_{DD} - I_{DQ} R_D) - (I_{DQ} R_S)$$

$$= (18 - (2.7 \times 10^{-3})(1500)) - ((2.7 \times 10^{-3})(750))$$

$$V_{DS} = 11.925 \text{ V} //$$

$$V_D = V_{DD} - I_{DQ} R_D$$

$$= 18 - (2.7 \times 10^{-3})(1500)$$

$$V_D = 13.95 \text{ V} //$$

- Since $I_B = 0$, thus

$$V_G = 0 \text{ V} //$$

while V_S can be evaluated as,

$$V_S = I_{DQ} R_S$$

$$= (2.7 \times 10^{-3})(750)$$

$$V_S = 2.025 \text{ V} //$$

7. Determine I_{DQ} for the network of fig. 6.72 using a purely mathematical approach. That is, establish a quadratic equation for I_D and choose the solution compatible with the network characteristics. Compare to the solution obtained in problem 6.

Recall Shockley's equation,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

Since $V_{GS} = -I_D R_S$, therefore,

$$I_D = I_{DSS} \left(1 + \frac{I_D R_S}{V_P}\right)^2$$

$$= 0,010 \left(1 + \frac{750 I_D}{-4}\right)^2$$


Solve the equation for I_D ,

$$I_D = 2,609 \text{ mA} \text{ OR } I_D = 10,9 \text{ mA}$$

$I_{DQ} = 2,609 \text{ mA}$, very close to $2,7 \text{ mA}$ calculated in problem 6.

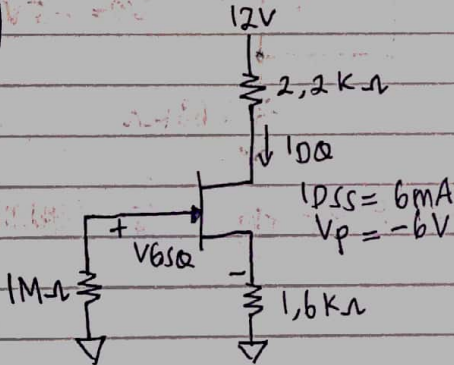8. for the network of Fig. 6.73. determine

- V_{GSQ} and I_{DQ}
- V_{DS} , V_D , V_G , and V_S



a) $V_{GS} = V_G - V_S$

$$V_{GS} = 0 - (1,6 I_D + 3)$$

$$V_{GS} = -1,6 I_D - 3$$

$$I_D = -\frac{V_{GS} + 3}{1,6} \quad \text{--- (1)}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\frac{V_{GS} + 3}{1,6} = 6 \left(1 - \frac{V_{GS}}{-6}\right)^2$$

$$-\frac{5}{8} V_{GS} - \frac{15}{8} = 6 + 2 V_{GS} + \frac{V_{GS}^2}{6}$$

$$\frac{V_{GS}^2}{6} + \frac{21}{8} V_{GS} + \frac{63}{8} = 0$$

Solving this quadratic equation,

$$V_{GS} = -4,03 \text{ V} \text{ OR } V_{GS} = -11,72 \text{ V}$$

(rejected $< V_P$)

$$V_{GSQ} = -4,03 \text{ V}$$

Substituting the value of V_{GSQ} in Eq. (1) gives.

$$I_{DQ} = -\frac{V_{GSQ} + 3}{1,6}$$

$$I_{DQ} = -\frac{-4,03 + 3}{1,6} = 643,75 \mu\text{A}$$

Thus, $V_{GSQ} \approx -4 \text{ V}$

$$I_{DQ} \approx 0,644 \text{ mA}$$

b) $V_D = 12 - 2,2 I_{DQ}$

$$= 12 - 2,2 \times 0,644 = 10,583 \text{ V}$$

$$V_S = 1,6 I_D + 3$$

$$= 1,6 \times 0,644 + 3 = 4,03 \text{ V}$$


Therefore,

$$V_{DS} = V_D - V_S$$

$$= 10,583 - 4,03$$

$$= 6,553 \text{ V}$$

$$V_G = 0$$

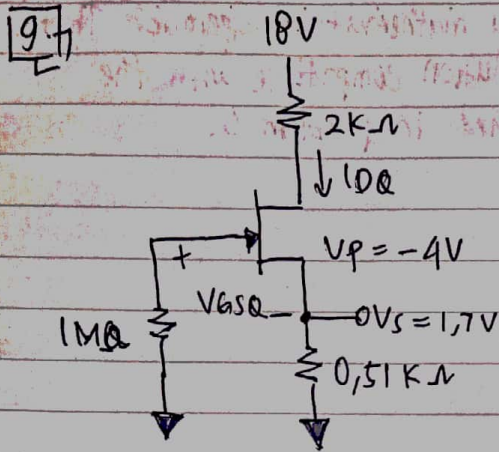

Given the measurement $V_s = 1.7V$, for the network of Fig. 6.74, determine:

- I_D
- V_{GSQ}
- I_{DSS}
- V_P
- V_{DS}

a.) $V_s = I_{DQ} \cdot R_S$

$$1.7 = I_{DQ} (510)$$

$$I_{DQ} = 3.33 \text{ mA}$$

b.) $V_{GSQ} = V_G - V_s$

while $V_G = 0V$, therefore,

$$V_{GSQ} = -V_s$$

$$V_{GSQ} = -1.7V //$$

c.) $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$

$$3.33 \times 10^{-3} = I_{DSS} \left(1 - \frac{-1.7}{-4} \right)^2$$

$$I_{DSS} = 10.07 \text{ mA} //$$

d.) $V_D = V_{DD} - I_D R_D$

$$= 18 - (3.33 \times 10^{-3} \times 2000)$$

$$V_D = 11.34V //$$

e.) $V_{DS} = V_D - V_s$

$$= 11.34 - 1.7$$

$$V_{DS} = 9.64V //$$

b.) Applying KVL to the loop that passes through the drain and source terminals gives

$$20 = 2.2 I_D + V_{DS} + 0.68 I_D - 4$$

$$20 = 2.2 \times 4.5 + V_{DS} + 0.68 \times 4.5 - 4$$

$$V_{DS} = 11.04V //$$


OR

$$V_{DS} = V_D - V_s$$

$$= 10.1 - (-0.94)$$

$$= 11.04V //$$

10.7

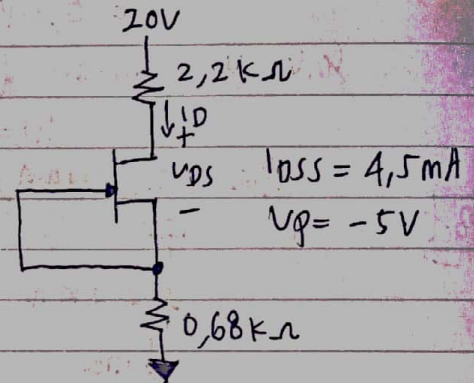

for the network of Fig. 6.75, determine

- I_D
- V_{DS}
- V_D
- V_s

a.) The gate terminal of the device is directly connected to the source terminal, thus $V_{GS} = 0$

$$I_D = I_{DSS} = 4.5 \text{ mA} //$$

c.) $V_D = 20 - 2.2 I_D$

$$= 20 - 2.2 \times 4.5$$


$$V_D = 10.1V //$$

d.) $V_s = 0.68 I_D - 4$

$$= 0.68 \times 4.5 - 4$$

$$V_s = -0.94V //$$

11.1

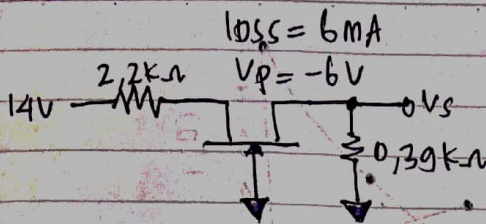find V_s for the network of Fig. 6.76.

$V_{GS} (V)$	$I_D (mA)$
0	$I_{DSS} = 6$
$0.3V_p = -1.8$	$\frac{I_{DSS}}{2} = 3$
$0.5V_p = -3$	$\frac{I_{DSS}}{4} = 1.5$
$V_p = -6$	0

$$V_{GS} = -I_D R_S ; \text{ for } I_D = 5 \text{ mA}$$

$$V_{GS} = -(0.005)(390)$$

$$V_{GS} = -1.95 \text{ V}$$


$$I_{DQ} = 3.55 \text{ mA}$$

$$V_{GSQ} = -1.4 \text{ V}$$


$$V_s = V_G - V_{GS}$$

$$= 0 - (-1.4)$$

$$V_s = 1.4 \text{ V} //$$

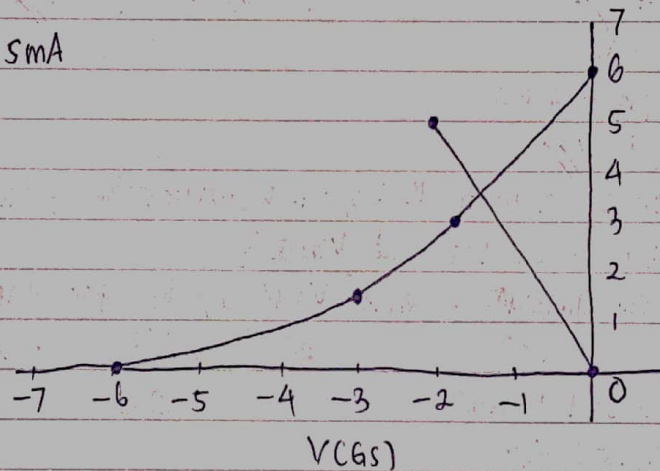

12.1

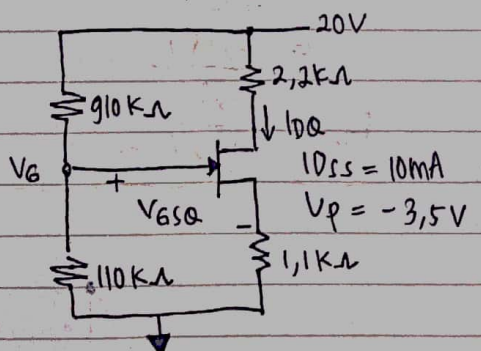

for the network of Fig. 6.11, Determine:

- V_G
- I_{DQ} and V_{GSQ}
- V_D and V_s
- V_{DSQ}

from voltage division at gate,

$$a.) V_G = \frac{110 \times 10^3}{110 \times 10^3 + 2.2 \times 10^3} (20)$$

$$V_G = 2.157 \text{ V} //$$

$V_{GS} (V)$	$I_D (mA)$
0	$I_{DSS} = 10$
$0.3V_p = -1.05$	$\frac{I_{DSS}}{2} = 5$
$0.5V_p = -1.75$	$\frac{I_{DSS}}{4} = 2.5$
$V_p = -3.5$	0

from the network equation,

$$V_{GS} = V_G - I_D R_S$$


$$= 2.157 - 1100 I_D \quad \text{--- (1)}$$

- for $I_D = 0 \text{ mA}$

$$\begin{aligned} V_{GS} &= 2,157 - (1100)(0) \\ &= 2,157 \text{ V} // \end{aligned}$$

- for $I_D = 4 \text{ mA}$
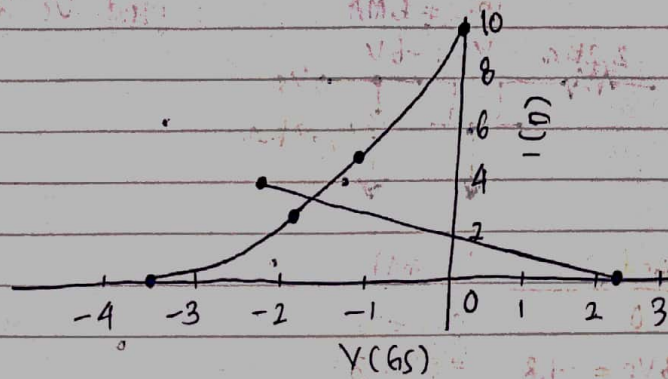
$$\begin{aligned} V_{GS} &= 2,157 - (1100)(0,004) \\ &= -2,243 \text{ V} // \end{aligned}$$



$$I_{DQ} = 3,3 \text{ mA} // \quad V_{GSQ} = -1,5 \text{ V} //$$

$$\begin{aligned} \text{c.) } V_D &= V_{DD} - I_D R_D \\ &= 20 - (0,0033)(2200) \\ V_D &= 12,74 \text{ V} // \end{aligned}$$

$$\begin{aligned} V_S &= I_D R_S \\ &= (0,0033)(1100) \\ V_S &= 3,63 \text{ V} // \end{aligned}$$

$$\begin{aligned} \text{d.) } V_{DS} &= V_D - V_S \\ &= 12,74 - 3,63 \\ V_{DSQ} &= 9,11 \text{ V} // \end{aligned}$$

13. a) repeat problem 12 with $R_S = 0,5 \text{ k}\Omega$ (about 50% of the value of 12). what is the effect of a smaller R_S on I_{DQ} and V_{GSQ} ?

b) what is the minimum possible value of R_S for the network of Fig. 1.71?

$$\begin{aligned} \text{a.) } V_G &= \frac{110 \times 10^3}{110 \times 10^3 + 910 \times 10^3} (20) \\ V_G &= 2,157 \text{ V} // \end{aligned}$$

$V_{GS} (\text{V})$	$I_D (\text{mA})$
0	$I_{DSS} = 10$
$0,3 V_P = -1,05$	$\frac{I_{DSS}}{2} = 5$
$0,5 V_P = -1,75$	$\frac{I_{DSS}}{4} = 2,5$
$V_P = -3,5$	0

b.) $R_S = \frac{V_S}{I_{DSS}}$; since $V_{GS} = 0$ at $I_D = I_{DSS}$ from Shockley's equation, therefore,

$$\begin{aligned} R_S &= \frac{V_G}{I_{DSS}} \\ &= \frac{2,157}{0,01} \end{aligned}$$


$$R_S = 215,7 \Omega //$$

$$\begin{aligned} V_{GS} &= V_G - I_D R_S \\ &= 2,157 - 510 I_D \dots \textcircled{1} \end{aligned}$$

- for $I_D = 0 \text{ mA}$ $\Rightarrow V_{GS} = 2,157 - (0)(510) = 2,157 \text{ V}$

- for $I_D = 7 \text{ mA}$ $\Rightarrow V_{GS} = 2,157 - (0,007)(510) = -1,413 \text{ V}$
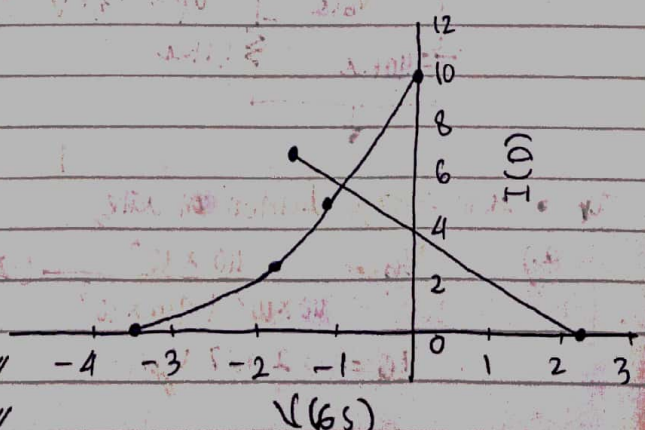
$$\begin{aligned} I_{DQ} &= 5,8 \text{ mA} \text{ (increased to almost the double)} // \\ V_{GSQ} &= -0,85 \text{ V} \text{ (Decreased to almost the half)} // \end{aligned}$$




$$\begin{aligned} V_D &= V_{DD} - I_D R_D \\ &= 20 - (0,0058)(2200) \\ V_D &= 7,24 \text{ V} // \end{aligned}$$

$$\begin{aligned} V_S &= I_D R_S \\ &= (0,0058)(510) \\ V_S &= 2,958 \text{ V} // \end{aligned}$$

$$\begin{aligned} V_{DS} &= V_D - V_S \\ &= 7,24 - 2,958 \\ V_{DSQ} &= 4,282 \text{ V} // \end{aligned}$$

14.7

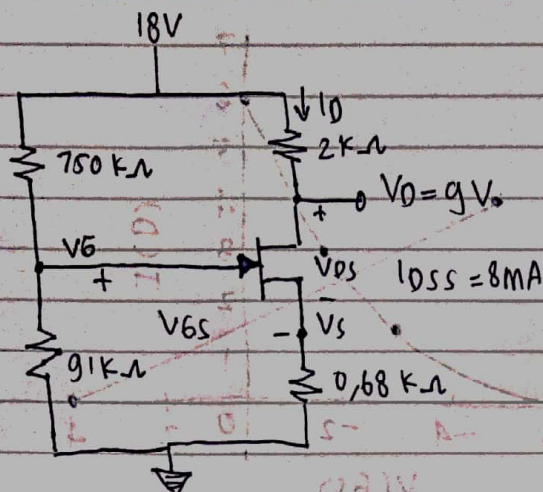for the network of fig. 6.78, $V_D = 9V$.

- I_D
- V_G and V_{GS}
- V_G and V_{GS}
- V_P

$$I_{DSS} = 8 \text{ mA}$$

$$V_{GS} = -3V$$

$$\begin{aligned} a.) I_D &= \frac{V_{DD} - V_D}{R_D} \\ &= \frac{18 - 9}{2000} = 4,5 \text{ mA} // \end{aligned}$$


$$\begin{aligned} b.) V_S &= I_D R_S \\ &= (0,0045)(750) \\ &= 3,375 \text{ V} // \\ V_{DS} &= V_D - V_S \\ &= 9 - 3,375 \\ &= 5,625 \text{ V} // \end{aligned}$$

$$c.) V_G = \frac{91 \times 10^3}{91 \times 10^3 + 750 \times 10^3} (18) = 1,947 \text{ V} //$$

$$\begin{aligned} V_{GS} &= V_G - V_S \\ &= 1,947 - 3,375 \\ &= -1,428 \text{ V} // \end{aligned}$$

$$\begin{aligned} d.) I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \\ 0,0045 &= 0,008 \left(1 - \frac{-1,428}{-3}\right)^2 \\ V_P &= \frac{-11 + \sqrt{73}}{3} \text{ V} \quad V_P = \frac{-11 - \sqrt{73}}{3} \text{ V} \\ &= -0,818 \text{ V} // \quad = -6,514 \text{ V} \end{aligned}$$

15.7

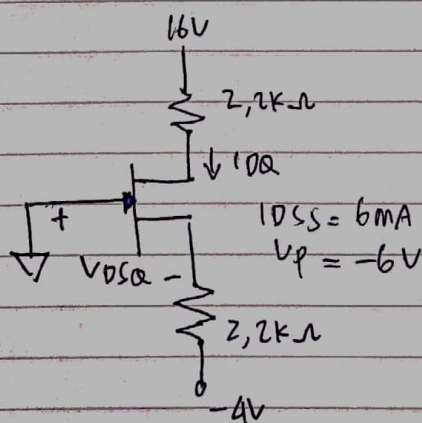

for the network of fig. 6.79, determine

- I_{DQ} and V_{GSQ}
- V_{PS} and V_S

$$\begin{aligned} V_{GS} &= V_G - (V_{SS} + I_D R_S) \\ &= 0 - (-4 + 2200 I_D) \\ &= 4 - 2200 I_D \dots \textcircled{1} \end{aligned}$$

$$\bullet \text{ for } I_D = 0 \text{ mA} \rightarrow V_{GS} = 4 - (0)(2200) = 4 \text{ V}$$


$$\bullet \text{ for } I_D = 4 \text{ mA} \rightarrow V_{GS} = 4 - (0,004)(2200) = -4,8 \text{ V}$$

$V_{GS} \text{ (V)}$	$I_D \text{ (mA)}$
0	$I_{DSS} = 6$
$0,3 V_P = -1,8$	$\frac{I_{DSS}}{2} = 3$
$0,5 V_P = -3$	$\frac{I_{DSS}}{4} = 1,5$
$V_P = -6$	0

- Sketch the transfer curve with the network equation superimposed on the same graph, from the intersection on figure 1

$$I_{DQ} = 2,7 \text{ mA} //$$

$$V_{GSQ} = -2 \text{ V} //$$

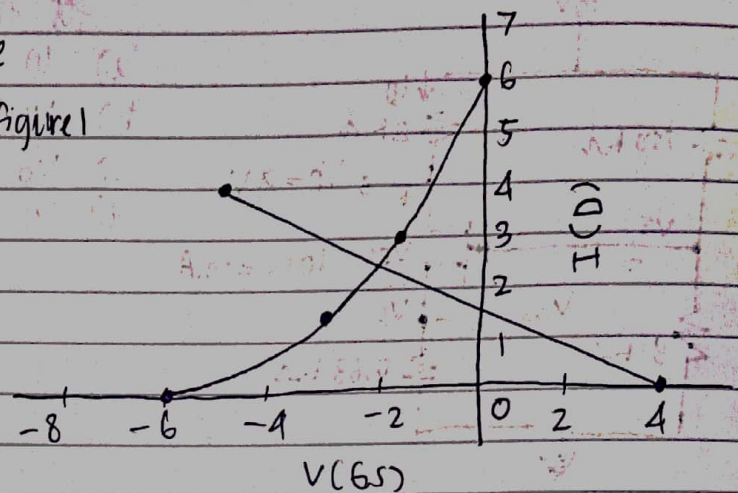

$$\begin{aligned} b.) V_S &= V_{SS} + I_{DQ} R_S \\ &= -4 + (0,0027)(2200) \\ &= 1,94 \text{ V} // \end{aligned}$$

$$\begin{aligned} V_{DS} &= V_D - V_S \\ &= (V_{DD} - I_{DQ} R_D) - V_S \\ &= (16 - 0,0027 \times 2200) - 1,94 \\ &= 8,12 \text{ V} // \end{aligned}$$