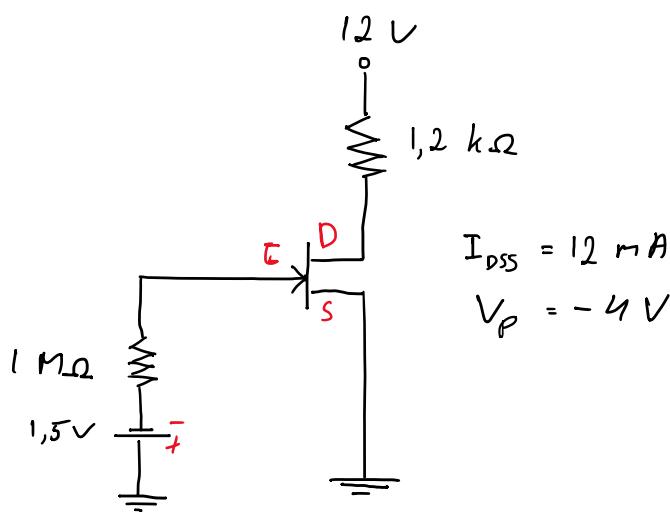


M. Hasyim Abdullah P.

1101101095


TT-93-11

1.




Fixed-Bias

a.

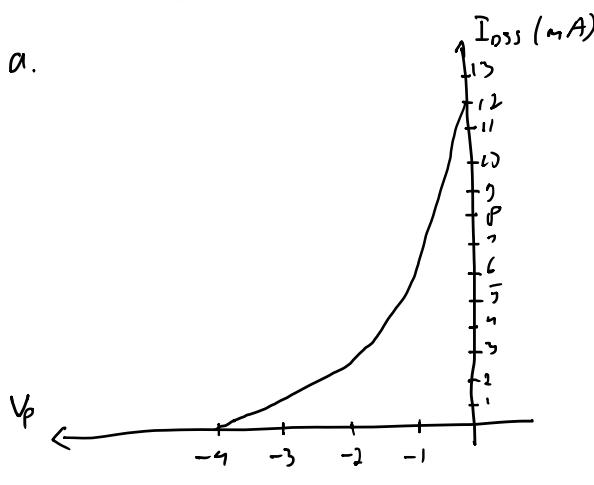

b.

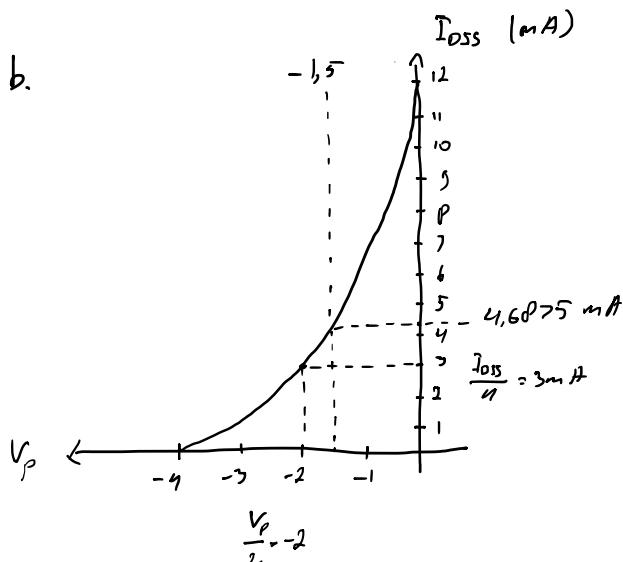


C.  $I_{DQ} = 4,6075 \text{ mA}$

$$\begin{aligned} V_{DSQ} &= V_{DD} - I_D R_D = 12 - 4,6075 \text{ mA} \cdot 1,2 \text{ k}\Omega \\ &= 12 - 5,625 \\ &= 6,375 \text{ V} \end{aligned}$$

$$\begin{aligned} d. \quad I_{DQ} &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \\ &= 12 \left(1 - \frac{-1,5}{-4}\right)^2 \\ &= 4,6075 \text{ mA} \end{aligned}$$

$$\begin{aligned} V_{DSQ} &= V_{DD} - I_{DQ} R_D \\ &= 12 - 4,6075 \text{ mA} \cdot 1,2 \text{ k}\Omega \\ &= 6,375 \text{ V} \end{aligned}$$

2.

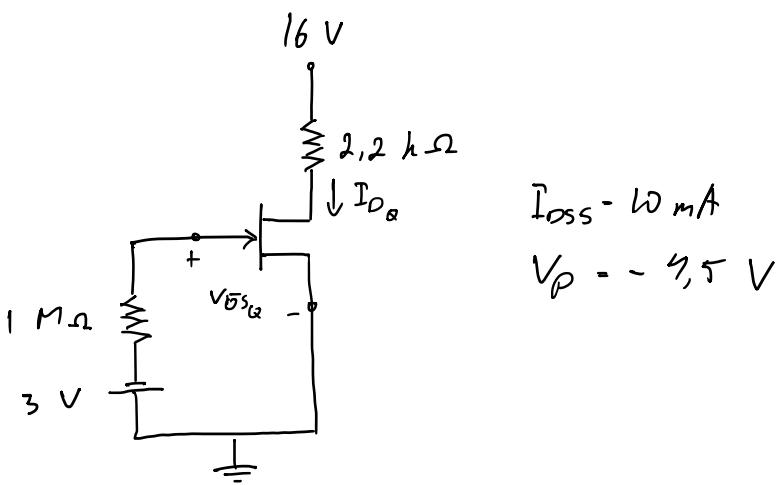


$$I_{DSS} = 60 \text{ mA}$$

$$V_P = -9.5 \text{ V}$$

$$a. \quad I_{DQ} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 = 60 \left( 1 - \frac{-3}{-9.5} \right)^2 = 1.11 \text{ mA}$$

$$V_{GSQ} = -V_{GG} = -3 \text{ V}$$

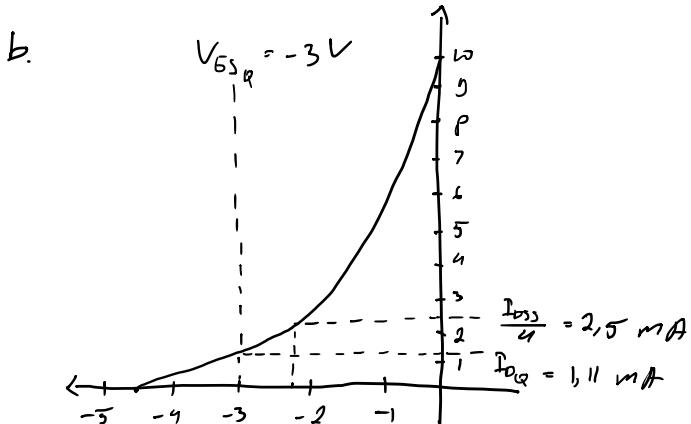

$$\frac{V_P}{2} = -2.25$$

$$c. \quad V_{DS} = V_{DD} - I_D R_D = 16 - 1.11 \text{ mA} \cdot 2.2 \text{ k}\Omega = 16 - 2.44 = 13.56 \text{ V}$$

$$V_{DS} = V_D - V_S$$

$\downarrow$   $\rightarrow I_D R_S$


$\boxed{V_{DD} - I_D R_D}$

$$V_D = V_{DS} = 13.56 \text{ V}$$

$$V_G = V_{GS} = -3 \text{ V}$$

$$V_S = 0 \text{ V}$$

3.

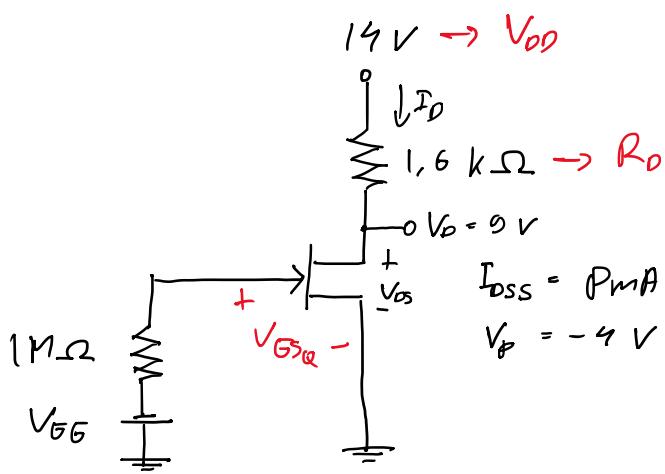

$$a. \quad V_D = V_{DD} - I_D R_D$$

$$0V = 14 - I_D \cdot 1,6 \text{ k}\Omega$$

$$I_D = \frac{5 \text{ V}}{1,6 \text{ k}\Omega} = 3,125 \text{ mA}$$

$$b. \quad V_{DS} = V_D - V_S$$

$$= 0 \text{ V} - 0$$

$$= 0 \text{ V}$$

$$c. \quad V_{GS} = -V_{GG}$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$\text{ES}$

$$3,125 = P \left( 1 - \frac{fV_{GG}}{fV_P} \right)^2$$

$$\frac{3,125}{P} = \sqrt{\frac{25}{64}} = \sqrt{\left( 1 - \frac{V_{GG}}{4} \right)^2}$$


$$\frac{5}{P} = 1 - \frac{V_{GG}}{4} \times 4$$

$$2,5 = 4 - V_{GG}$$

$$V_{GG} = 1,5 \text{ V}$$

~~$$V_{GG} = 1,76 \text{ V}$$~~

4.

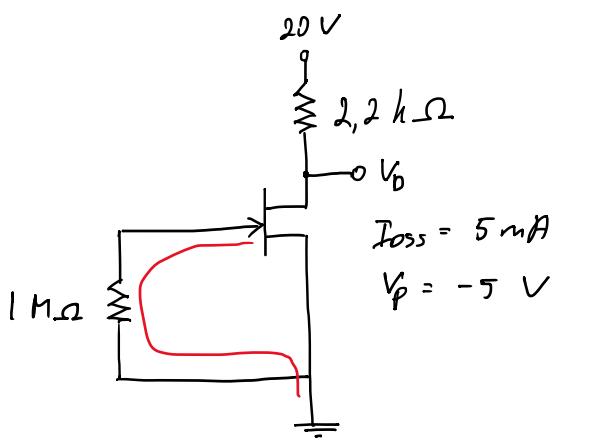

$$I_D = I_{DSS} \left(1 - \frac{V_{DS}}{V_P}\right)^2$$


$$I_D = 5 \text{ mA} \left(1 - \frac{0}{-5}\right)^2$$

$$I_D = 5 \text{ mA}$$

$$V_D = V_{DD} - I_D R_D = 20 - 5 \text{ mA} \cdot 2.2 \text{ k}\Omega$$
 $\Rightarrow 20 - 11$

$$= 9 \text{ V}$$

5.

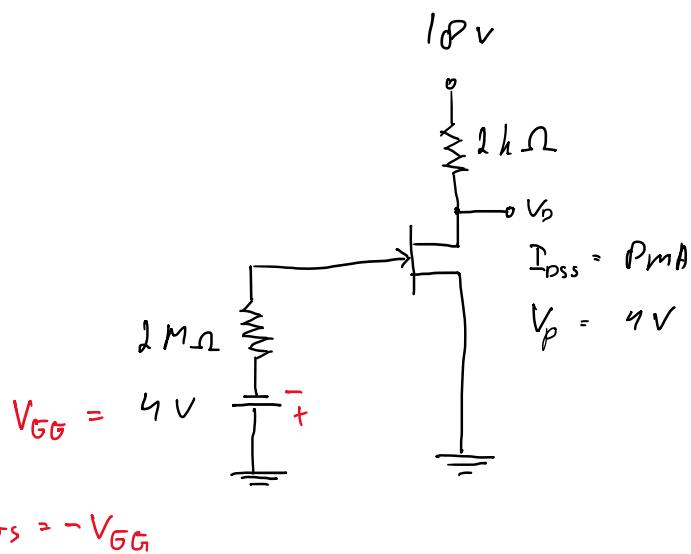

$$I_D = I_{DSS} \left(1 - \frac{V_{DS}}{V_P}\right)^2$$

$$I_D = 32 \text{ mA} \left(1 - \frac{-4}{4}\right)^2$$

$$I_D = 32 \text{ mA} \cdot 4$$

$$I_D = 128 \text{ mA}$$

$$V_D = V_{DD} - I_D R_D$$


$$= 10 - 128 \text{ mA} \cdot 2 \text{ k}\Omega$$

$$= -46 \text{ V}$$


$$I_D = 32 \text{ mA} \left(1 - \frac{-4}{-4}\right)^2$$

$$I_D = 0 \rightarrow V_D = V_{DD} - \cancel{I_D R_D} = V_{DD} = 10 \text{ V}$$


6.

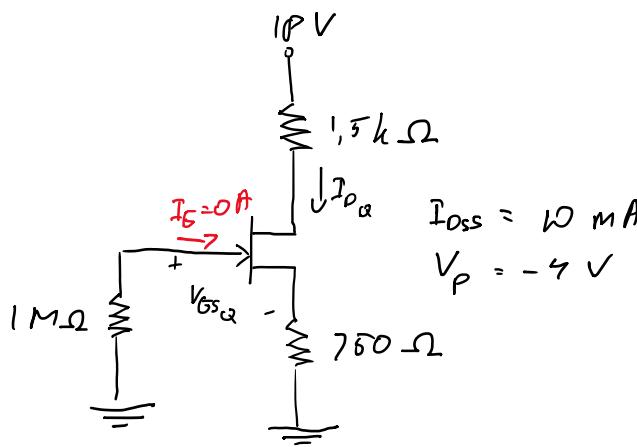

a.

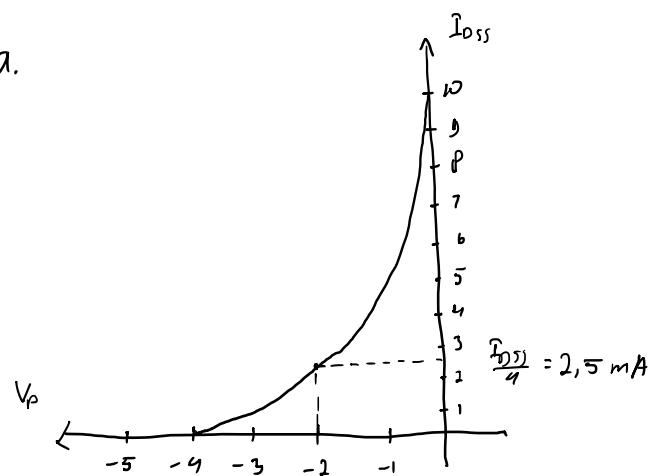Self-Bias

b.

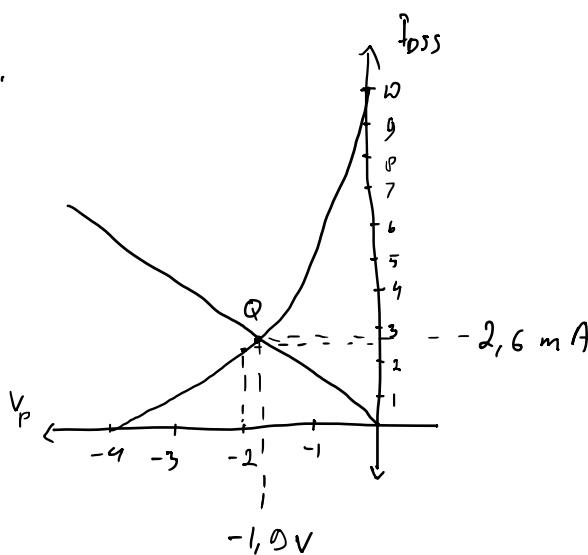

$$d. V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$= 10 - 2.6 \text{ mA}(1.5 \text{ k}\Omega + 750 \text{ }\Omega)$$

$$= 10 - 5.05$$

$$= 12.15 \text{ V}$$

$$V_D = V_{DD} - I_D R_D$$

$$= 10 - 2.6 \text{ mA} \cdot 1.5 \text{ k}\Omega$$

$$= 10 - 3.9$$

$$= 14.1 \text{ V}$$

$$V_G = 0 \text{ V}$$

$$c. I_{DQ} = 2.6 \text{ mA}$$

$$V_{GSQ} = V_{GS} - I_D R_S$$

$$V_{GS} = -I_D R_S$$

$$V_{GSQ} = -1.0 \text{ V}$$

$$I_D = I_{DSs} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = I_{DSs} \left( 1 - \frac{-I_D R_S}{V_P} \right)^2$$

$$AI_D^2 + BI_D + C = 0$$

$$V_{DS} = V_D - V_S$$


$$I_{D,2} \rightarrow I_D \leq I_{DSs} \&$$

$$12.15 = 14.1 - V_S$$

$$V_{GS} \geq V_P$$

$$V_S = 1.95 \text{ V}$$

7.

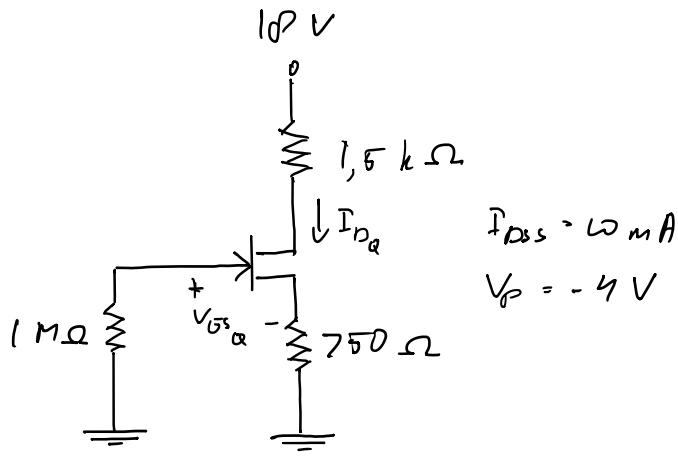

$$I_{DSS} = 10 \text{ mA}$$

$$V_P = -4 \text{ V}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_D = 10 \text{ mA} \left(1 - \frac{V_{GS}}{-4 \text{ V}}\right)^2 \leftarrow V_{GS} = -I_D R_S$$

$$I_D = 0,01 \text{ A} \left(1 - \frac{-I_D R_S}{-4 \text{ V}}\right)^2$$

$$I_D = 0,01 \left(1 - \frac{I_D \cdot 750}{4}\right)^2$$

$$I_D = \frac{1}{150} \left(1 - \frac{375 I_D}{2}\right)^2$$

$$I_D = \frac{1}{150} \left(\frac{2 - 375 I_D}{2}\right)^2$$

$$I_D = \frac{(2 - 375 I_D)^2}{150 \cdot 2^2}$$

$$I_D = \frac{4 - 1500 I_D + 375^2 I_D^2}{400}$$


$$400 I_D = 4 - 1500 I_D + 375^2 I_D^2$$

$$375^2 I_D^2 - 1500 I_D + 4 = 0$$

$$I_{D,1,2} = \frac{1500 \pm \sqrt{1500^2 - 4 \cdot 375^2 \cdot 4}}{2 \cdot 375^2}$$

$$I_{D_1} = 2,61 \text{ mA} \longrightarrow I_{D_Q} = I_{D_1} = 2,61 \text{ mA} \quad (\cancel{I_{D_Q} \leq I_{DSS} \text{ dan } V_{GS} \geq V_P})$$

$$I_{D_2} = 10,0 \text{ mA} \quad X$$

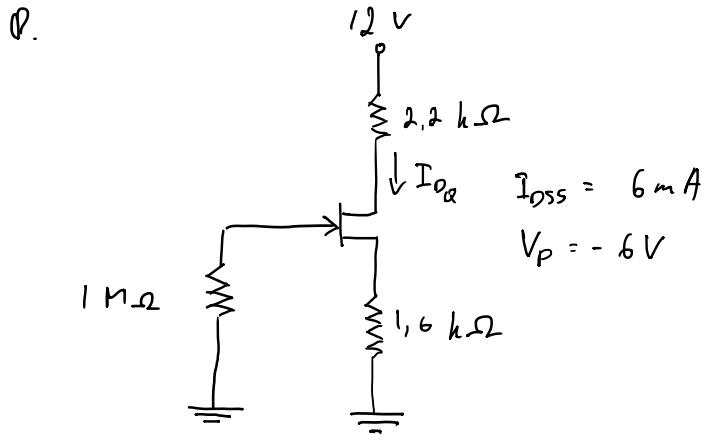

$$a. \quad V_{DS} = -I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{DS}}{V_P}\right)^2$$

$$I_D = I_{DSS} \left(1 - \frac{-I_D R_S}{V_P}\right)^2$$

$$I_D = 6 \text{ mA} \left(1 - \frac{-I_D \cdot 1.6 \text{ k}\Omega}{-6 \text{ V}}\right)^2$$

$$I_D = 0.006 \text{ A} \left(1 - \frac{800 I_D}{3}\right)^2$$

$$I_D = \frac{6}{800} \left(\frac{3 - 800 I_D}{3}\right)^2$$

$$I_D = \frac{6(3 - 800 I_D)^2}{800 \cdot 3^2}$$

$$I_D = \frac{9 - 4800 I_D + 800^2 I_D^2}{1500}$$

$$800^2 I_D^2 - 6300 I_D + 9 = 0$$

$$I_D = \frac{6300 \pm \sqrt{6300^2 - 4 \cdot 800^2 \cdot 9}}{2 \cdot 800^2}$$

$$I_{D_1} = 1.73 \text{ mA}$$

$$I_{D_2} = 0.11 \text{ mA}$$

$$I_{D_Q} = I_D = 1.73 \text{ mA}$$

$$V_{GSQ} = -I_D \cdot R_S$$

$$= -1.73 \text{ mA} \cdot 1.6 \text{ k}\Omega$$

$$= -2.76 \text{ V}$$

$$b. \quad V_D = V_{DS} - I_D (R_D + R_S)$$

$$= 12 - 1.73 \text{ mA} (2.2 \text{ k}\Omega + 1.6 \text{ k}\Omega)$$

$$= 12 - 6.574$$

$$= 5.426 \text{ V}$$

$$V_D = V_{DS} - I_D R_D$$

$$= 12 - 1.73 \text{ mA} \cdot 2.2 \text{ k}\Omega$$

$$= 8.194 \text{ V}$$

$$V_G = 0 \text{ V}$$


$$V_S = V_G - V_{DS}$$

$$= 0 - (-2.76 \text{ V})$$

$$= 2.76 \text{ V}$$

$$V_{GS} = V_G - V_S$$

$$V_S = V_G - V_{DS}$$

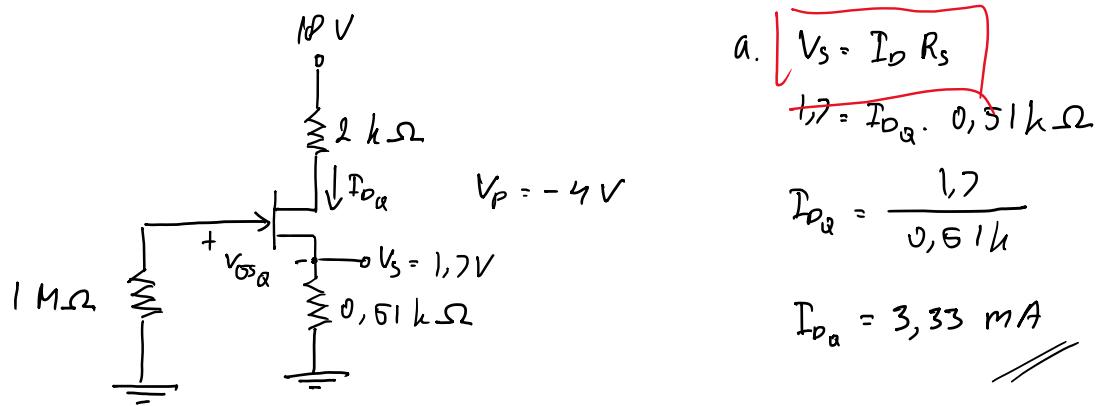

a.  $V_S = I_D R_S$

$$1,7 = I_{DQ} \cdot 0,51 \text{ k}\Omega$$

$$I_{DQ} = \frac{1,7}{0,51 \text{ k}\Omega}$$

$$I_{DQ} = 3,33 \text{ mA}$$

b.  $V_{GSQ} = -I_D R_S = -V_S = -1,7 \text{ V}$

c.  $I_{DQ} = I_{DSS} \left(1 - \frac{V_{GSQ}}{V_P}\right)^2$

$$3,33 \text{ mA} = I_{DSS} \left(1 - \frac{-1,7}{-4}\right)^2$$

$$I_{DSS} = \frac{3,33}{\left(1 - \frac{1,7}{4}\right)^2}$$

$I_{DSS} = 10 \text{ mA}$

d.  $V_D = V_{DD} - I_D R_D$


$$V_D = 10 - 3,33 \text{ mA} \cdot 2 \text{ k}\Omega$$

$$V_D = 11,34 \text{ V}$$

e.  $V_{DS} = V_D - V_S$

$$= 11,34 - 1,7$$

$$= 9,64 \text{ V}$$

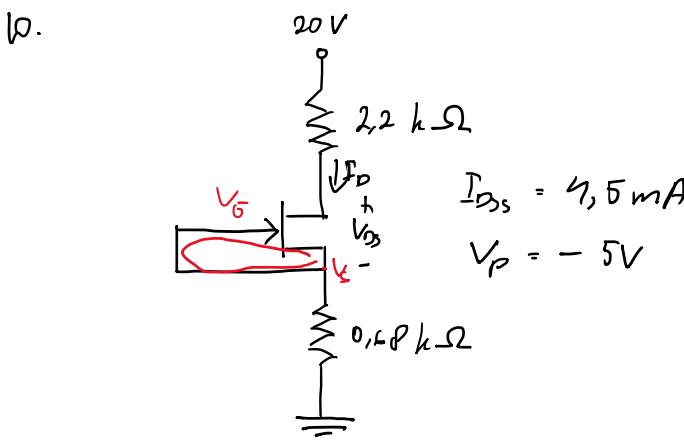

a.  $V_{DS} = -I_D R_S = 0 \checkmark$

$$I_D = I_{DS} \left(1 - \frac{V_{DS}}{V_P}\right)^2$$

$$I_D = I_{DS} \left(1 - \frac{0}{-5V}\right)^2$$

$$I_D = 4.5 \text{ mA} \left(1 - \frac{0}{-5V}\right)^2$$

$$\cancel{I_D = 4.5 \text{ mA}}$$

b.  $V_{DS} = V_{DD} - I_D (R_D + R_S)$

$$V_{DS} = 20 - 4.5 \text{ mA} (2.2 \text{ k}\Omega + 0.6 \text{ k}\Omega)$$

$$V_{DS} = 20 - 12.06$$

$$\cancel{V_{DS} = 7.04 \text{ V}}$$

$$V_{DS} > V_D - V_S \Rightarrow V_D = V_S$$

$$V_{DS} = 0$$

c.  $V_D = V_{DD} - I_D R_D$

$$= 20 - 4.5 \text{ mA} \cdot 2.2 \text{ k}\Omega$$

$$= 20 - 9.9$$


$$= 10.1 \checkmark$$

d.  $V_{DS} = V_D - V_S$

$$V_S = V_D - V_{DS}$$

$$V_S = 10.1 - 7.04$$

$$V_S = 3.06 \text{ V}$$

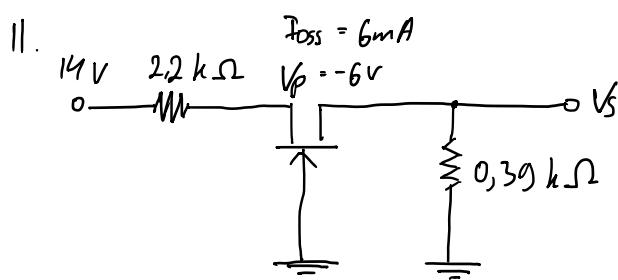

$$V_{GS} = -I_D R_S$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = 6 \text{ mA} \left( 1 - \frac{-I_D R_S}{-6 \text{ V}} \right)^2$$

$$I_D = \frac{6}{1000} \text{ A} \left( 1 - \frac{I_D \cdot 0.39}{6} \right)^2$$

$$\frac{I_D}{I_D} = \frac{3}{500} \left( 1 - 65 I_D \right)^2$$

$$\frac{500}{3} I_D = 1 - 130 I_D + 65^2 I_D^2$$

$$500 I_D = 3 - 390 I_D + 3.65^2 I_D^2$$

$$12675 I_D^2 - 820 I_D + 3 = 0$$

$$I_{D1,2} = \frac{820 \pm \sqrt{820^2 - 4 \cdot 12675 \cdot 3}}{2 \cdot 12675}$$

$$I_{D1} = 66.67 \text{ mA}$$

$$I_{D2} = 3.55 \text{ mA}$$

$$I_{DQ} = I_{D2} = 3.55 \text{ mA}$$


$$V_{GS} = -I_D R_S$$

$$V_G - V_S = -3.55 \text{ mA} \cdot 0.39 \text{ k}\Omega$$


$$0 - V_S = -1.3845 \text{ V}$$

$$V_S = 1.3845 \text{ V}$$

Common Gate

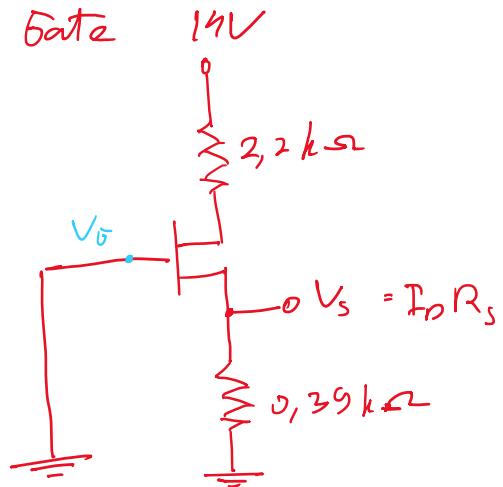

12.

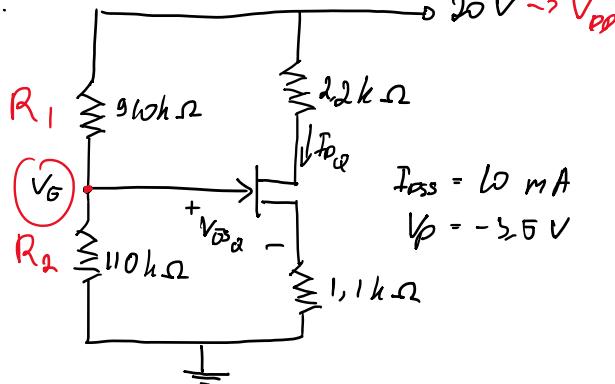

Voltage Divider - Bias

$$a. \quad V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$V_G = \frac{110k}{960h + 110k} \cdot 20V$$

$$V_G = \frac{110k}{1020k} \cdot 20V$$

$$V_G = 2,16V$$

$$b. \quad V_{GS} = V_G - (I_D R_S)$$

$$V_{GS} = 2,16 - I_D \cdot 1,1k\Omega$$

$$I_D = I_{DSs} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = 10mA \left( 1 - \frac{2,16 - 1100I_D}{-3,5} \right)^2$$

$$I_D = \frac{1}{100} A \left( \frac{3,5}{3,5} + \frac{2,16 - 1100I_D}{3,5} \right)^2$$

$$I_D = \frac{(5,66 - 1100I_D)^2}{100 \cdot 3,5^2}$$

$$1225I_D^2 = 32,04 - 12452I_D + 1100^2 I_D^2$$

$$1100^2 I_D^2 - 13677I_D + 32,04 = 0$$

$$I_{D,1,2} = \frac{13677 \pm \sqrt{13677^2 - 4 \cdot 1100^2 \cdot 32,04}}{2 \cdot 1100^2}$$

$$I_{D1} = 7,09mA$$

$$V_{GS1} = 2,16 - 3,31mA \cdot 1,1k\Omega$$

$$V_{GS1} = -1401V$$

$$I_{D2} = 3,31mA \rightarrow I_{DQ} = 3,31mA$$

$$V_{GSQ} = 2,16 - I_D \cdot 1,1k\Omega$$

$$V_{GSQ} = 2,16 - 3,31mA \cdot 1,1k\Omega$$

$$\underline{\underline{V_{GSQ} = -1,40V}}$$

$$c. \quad V_D = V_{DD} - I_D R_D$$

$$V_D = 20 - 3,31mA \cdot 2,2k\Omega$$

$$V_D = 12,71V$$

$$V_S = I_D R_S$$

$$V_S = 3,31mA \cdot 1,1k\Omega$$

$$V_S = 3,641V$$


$$d. \quad V_{DSQ} = V_D - V_S$$

$$V_{DSQ} = 12,71V - 3,641$$

$$\underline{\underline{V_{DSQ} = 9,077V}}$$

$$V_{GS1} = 2,16 - 3,31mA \cdot 1,1k\Omega$$

$$V_{GS1} = -6,61V$$

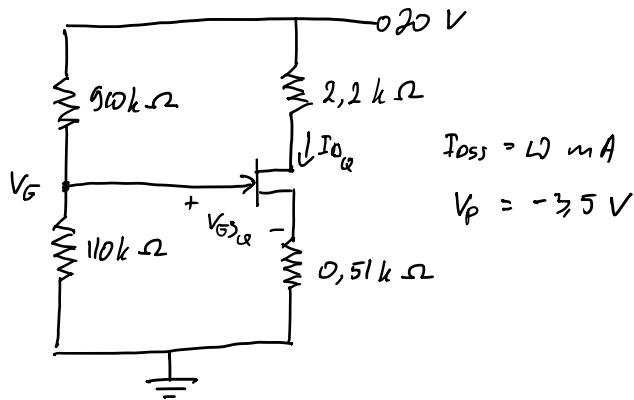

$$a. V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$V_G = \frac{110k}{50k + 110k} 20V$$

$$V_G = 2.16 V$$

$$V_{G-S_Q} > V_G - I_D R_S$$

$$V_{GS} = 2.16 - I_D \cdot 0.51k \Omega$$

$$I_D = I_{DS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_D = 10mA \left(1 - \frac{2.16 - 510I_D}{-3.5}\right)^2$$

$$25500^2 I_D^2 - 17495500 I_D + 1000000 = 0$$

$$I_{D1} = 21.06 mA$$

$$I_{D2} = 5.85 mA$$

$$I_{DQ} = 5.85 mA$$

$$V_{GSQ} = 2.16 - I_D \cdot 0.51k \Omega$$


$$V_{GSQ} = 2.16 - 5.85mA \cdot 0.51k \Omega$$

$$V_{GSQ} = -0.8235 V$$

b. Nilai minimum dari  $R_S$  adalah  $0 \Omega$

$\therefore$  semakin kecil nilai  $R_S$  maka semakin besar nilai  $I_{DQ}$  dan  $V_{GSQ}$

14.

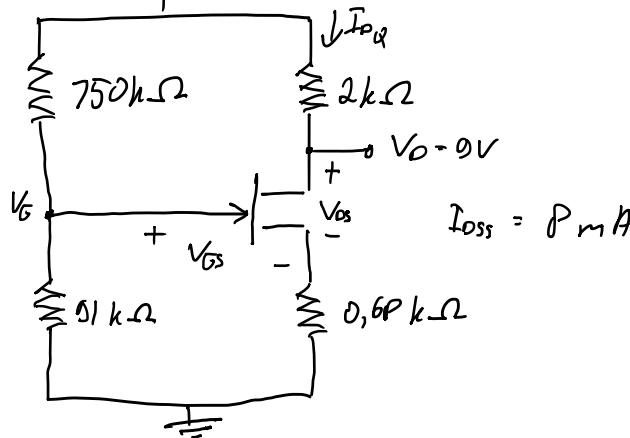

$$b. V_S = I_D R_S$$

$$V_S = 4.5 \text{ mA} \cdot 0.6P \text{ k}\Omega$$

$$V_S = 3.06 \text{ V}$$

$$V_{DS} = V_D - V_S$$

$$V_{DS} = 0 - 3.06$$

$$V_{GS} = 5.94 \text{ V}$$

$$c. V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$V_G = \frac{91\text{k}}{750\text{k} + 91\text{k}} \cdot 18$$

$$V_G = \frac{91\text{k}}{841\text{k}} \cdot 18$$

$$V_G = 1.95 \text{ V}$$

$$V_{GS} = V_G - V_S$$

$$= 1.95 - 3.06$$

$$= -1.11 \text{ V}$$

$$d. V_D = V_{DD} - I_D R_D$$

$$0 = 18 - I_D \cdot 2k\Omega$$

$$I_D = \frac{0}{2k\Omega}$$

$$I_D = 4.5 \text{ mA}$$

d.

$$I_D = I_{LOSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$4.5 \text{ mA} = P_{mA} \left( 1 - \frac{-1.11 \text{ V}}{V_P} \right)^2$$

$$4.5 = P \left( 1 + \frac{1.11}{100V_P} \right)^2$$

$$4.5 = P \left( \frac{100V_P + 1.11}{100V_P} \right)^2$$

$$4.5 = P \frac{(100V_P + 1.11)^2}{10000V_P^2}$$

$$5625V_P^2 = 10000V_P^2 + 22200V_P + 12321$$

$$4375V_P^2 + 22200V_P + 12321 = 0$$


$$V_{P_{1,2}} = \frac{-22200 \pm \sqrt{22200^2 - 4 \cdot 4375 \cdot 12321}}{2 \cdot 4375}$$

$$V_{P_1} = -0.63 \text{ V}$$

$$V_{P_2} = -4.44 \text{ V}$$

$$(V_P \leq V_{GSQ})$$
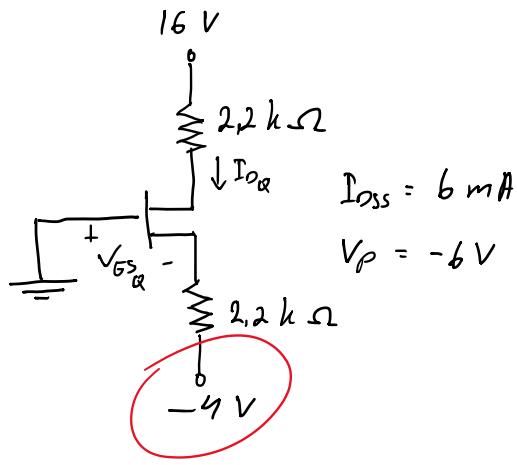
$$\therefore V_P = V_{P_2} = -4.44 \text{ V}$$



Common Gate

$$V_{GS} = V_G - V_S - V_{SS}$$

$$a. V_{GS} = -V_{SS} - I_D R_s$$

$$V_{GS} = -(-4) - I_D \cdot 2,2k\Omega$$

$$V_{GS} = 4 - I_D \cdot 2,2k\Omega$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2$$

$$I_D = 6mA \left( 1 - \frac{4 - 2200I_D}{-6} \right)^2$$

$$I_D = \frac{6}{1000} \left( 1 + \frac{2 - 1100I_D}{3} \right)^2$$

$$I_D = \frac{3}{500} \left( \frac{5 - 1100I_D}{3} \right)^2$$

$$I_D = \frac{3(5 - 1100I_D)}{500 \cdot 3^2}^2$$

$$1500I_D = 25 - 1100I_D + 1100^2 I_D^2$$

$$1100^2 I_D^2 - 12500I_D + 25 = 0$$

$$I_{D,1,2} = \frac{12500 \pm \sqrt{12500^2 - 4 \cdot 1100^2 \cdot 25}}{2 \cdot 1100^2}$$

$$I_{D_1} = 7,62 \text{ mA}$$

$$I_{D_2} = 2,71 \text{ mA}$$

$$I_{D_Q} < I_{DSS} \Rightarrow I_{D_Q} = 2,71 \text{ mA}$$

$$V_{GSQ} = 4 - 2,71 \text{ mA} \cdot 2,2k\Omega$$

$$= -1,062 \text{ V}$$

$$b. V_{DS} = V_D - V_S - I_D (R_D + R_s)$$

$$= 16 - (-4) - 2,71 \text{ mA} (2,2k\Omega + 2,2k\Omega)$$

$$= 20 - 11,924$$

$$= 8,076 \text{ V}$$

$$V_S = I_D R_s$$

$$= 2,71 \text{ mA} \cdot 2,2k\Omega$$

$$= 5,962 \text{ V}$$