
M. Hasyim Abdillah P. 1101191095

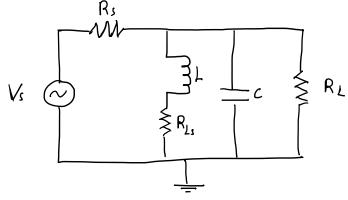

$$f_{\Gamma} = \frac{1}{2\pi\sqrt{1c}}$$


$$120 \times 10^6 = \frac{1}{2\pi \sqrt{40 \times 10^{-9} \cdot C}}$$

$$120^{2} \times 10^{12} = \frac{1}{4 \pi^{2}, 40 \times 10^{-9}. C}$$

$$\mathcal{L}. \qquad Q = \frac{X_s}{R_{ls}}$$

$$R_{Lp} = R_{Ls} \left( Q^2 + l \right)$$

$$R_{LP} = 3 k \Omega$$

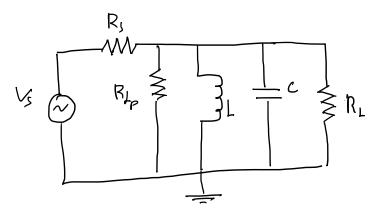

$$\frac{1}{R_p} = \frac{1}{50} + \frac{1}{50} + \frac{1}{3000}$$

$$Q_{T} = \frac{R_{P}}{\times_{P}} = \frac{24,79}{2E \cdot f_{F} \cdot L}$$

$$Q_{T} = \frac{24,79}{2E \cdot 120 \times 10^{2} \cdot 40 \times 10^{2}}$$

e. 
$$R_2 = \frac{R_{4p} \cdot R_4}{R_{4p} + R_1} = \frac{3000.57}{3000 + 50} = 49, 19 = 0$$

$$V_1 = \frac{R_2}{R_S + R_Z}$$
  $V_S = \frac{49.10}{50 + 49.10}$   $V_S = 0, 496 V_S$ 

$$V_1 = \frac{R_4}{R_1 + R_2} \cdot V_2 = \frac{50}{50 + 50} V_5 = 0,5 V_5$$

Insertion Loss = 10 log 
$$\left(\frac{V_L}{V_L}\right)$$
  
= 10 log  $\left(\frac{5 \times 10^{-3} \text{ Vs}}{7,92 \times 10^{-3} \text{ Vs}^2}\right)$